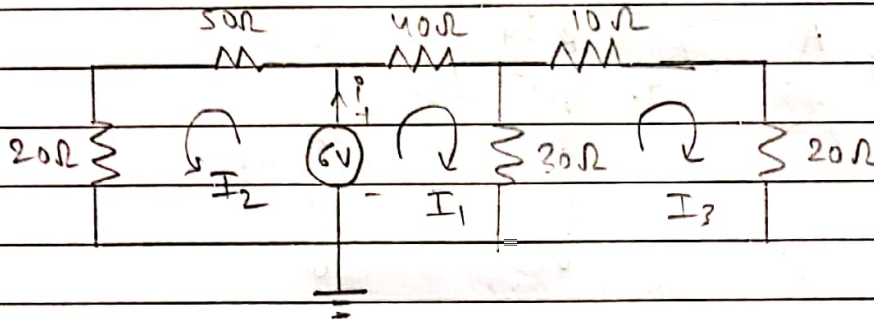


Q.2.

A.

9



→

Consider loop 1.

By Applying KVL law:-

$$6 - 40(I_1) - 30(I_1 - I_2) = 0$$

$$6 - 70I_1 + 30I_2 = 0$$

$$70I_1 - 30I_2 = 6 \rightarrow (1)$$

Consider loop 2.

By Applying KVL law:-

$$6 - 50(I_2) - 20(I_2) = 0$$

$$6 = 70I_2$$

$$I_2 = 0.086 \text{ Amp} \rightarrow (2)$$

Consider loop 3.

By Applying KVL law:-

$$-30(I_3 - I_1) - 10(I_3) - 20(I_3) = 0$$

$$30I_1 = 60I_3$$

$$I_1 = 2I_3 \rightarrow (3)$$

Put (3) in (1)

$$70 \times 2I_3 - 30I_3 = 6$$

$$I_3 = 0.055 \text{ Amp} \rightarrow (4)$$

Put (4) in (1)

$$\therefore 70 I_1 - 30 \times 0.055 = 6$$

$$\therefore I_1 = 0.109 \text{ Amp} \rightarrow (5)$$


$$\begin{aligned} \therefore \text{Current } i &= I_1 + I_2 \\ &= 0.109 + 0.086 \\ &= 0.195 \text{ Amp} \uparrow \end{aligned}$$

Ans:- Current  $i$  through 6 V is 0.195 Amp  $\uparrow$

iii

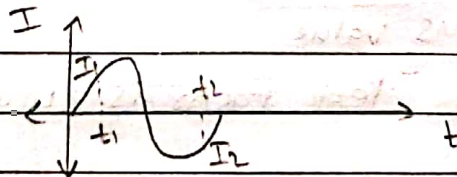(A) Instantaneous Value:-

→ The value of an alternating current (A.C) quantity at a given time instance is known as its instantaneous value. eg. Let  $I_1, I_2$  be instantaneous current values at time  $t_1, t_2$



(B) RMS Value:-

→ The value of AC changes with time, whereas the D.C quantity for same conditions remains constant with time. The rms value is the criteria to measure the effective A.C value.

The effective rms value of an A.C is equal to that D.C value which when flowing through a given resistance for a given period of time produces the same amount



of heat or work done as that when the A.C value was flowing through the circuit.

RMS Value = Root Mean Square Value

(C) Form Factor

→ It is the ratio of RMS value to the average value of an A.C quantity.

$$\text{Form factor} = \frac{\text{RMS Value}}{\text{Average Value}}$$

For a Sine Wave Form factor is 1.11

(D) Peak Factor

→ It is the ratio of Maximum value to the rms value of an A.C quantity.


$$\text{Peak Factor} = \frac{\text{Maximum Value}}{\text{RMS Value}}$$

For a Sine Wave Peak Factor is 1.414

2. (B)

(i)

→

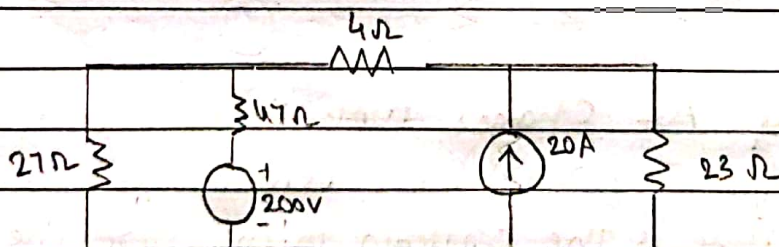


Yash. P. Dalvi  
7128402  
Ydalvi

BEE

4/15

Case 1:- Consider 200V supply source

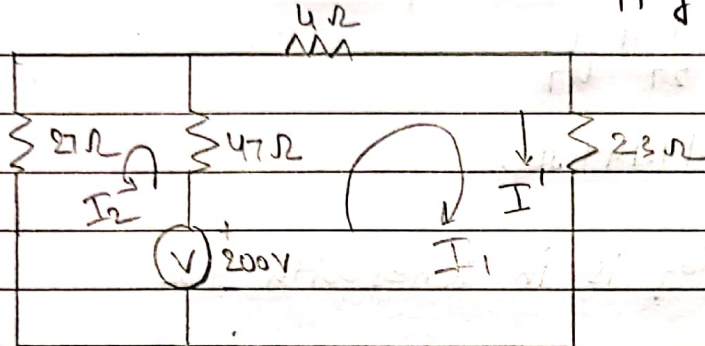

In loop 1.

Applying KVL Law:-

$$200 - 47(I_1 + I_2) - 4(I_1) - 23(I_1) = 0$$

$$\therefore 74 I_1 + 47 I_2 = 200 \rightarrow (1)$$

In loop 2.

Applying KVL Law:-

$$200 - 47(I_2 + I_1) - 27(I_2) = 0$$


$$\therefore 47 I_1 + 74 I_2 = 200 \rightarrow (2)$$

Solving (1) and (2) - simultaneously we get

$$I_1 = 1.653 \text{ Amp} ; I_2 = 1.653 \text{ Amp}$$

$$\therefore I_{23} = I' = 1.653 \downarrow$$

Case 2:- Considering 20 A supply source.

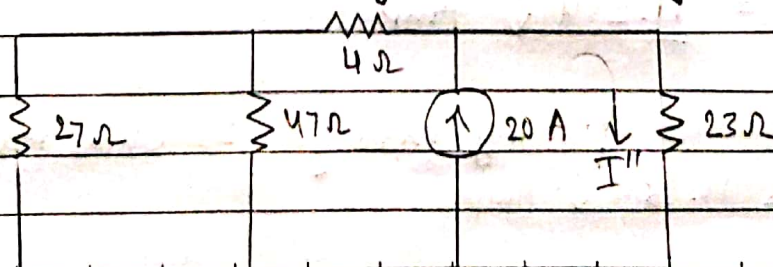



$\therefore 27\Omega$  and  $47\Omega$  are in parallel.

$$\therefore \frac{1}{R_{eq}} = \frac{1}{27} + \frac{1}{47}$$


$$\therefore R_{eq} = 17.149\Omega$$

Now, this  $R_{eq}$  is in series with  $4\Omega$

$$\therefore R''_{eq} = R_{eq} + 4$$
$$= 17.149 + 4$$

$$R''_{eq} = 21.149\Omega$$

New diagram is :-

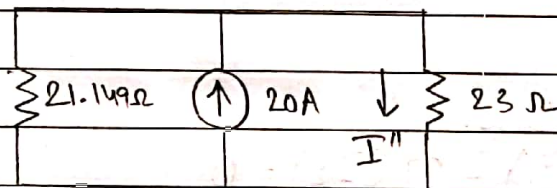

$\therefore$  By Current Divider Formula.

$$I'' = \frac{20 \times 21.149}{21.149 + 23} = 9.581 \text{ Amp} \downarrow$$

By Super position theorem.

$$I_{23} = I' + I''$$
$$= 1.653 + 9.581$$

$$I_{23} = 11.234 \downarrow \text{ Amp}$$

Ans:- Current flowing through  $23\Omega$  resistance  
is  $11.234 \downarrow \text{ Amp}$